


# HIERARCHICAL DESIGN

## Outline

1. Introduction
2. Components
3. Generics
4. Configuration
5. Other supporting constructs
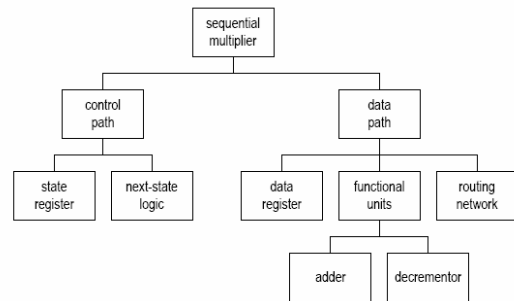
## 1. Introduction

- How to deal with 1M gates or more?
- Hierarchical design
  - Divided-and-conquer strategy
  - Divide a system into smaller parts



## Benefits of hierarchical design

- Complexity management
  - Focus on a manageable portion of the system, and analyze, design and verify each module in isolation.
  - Construct the system in stages by a designer or concurrently by a team of designers.
  - Help synthesis process
- Design reuse
  - Use predesigned modules or third-party cores
  - Use the same module in different design
  - Isolate device-dependent components (e.g., SRAM)

## Relevant VHDL constructs

- Component
- Generic
- Configuration
- Library
- Package
- Subprogram

## 2. Components

- Hierarchical design usually shown as a block diagram (structural description)
- VHDL component is the mechanism to describe structural description in text
- To use a component
  - Component declaration (make known)
  - Component instantiation (create an instance)

## Component declaration

- In the declaration section of entity
- Info similar to entity declaration
- Syntax:

```

component component_name
  generic (
    generic_declaration;
    generic_declaration;
    . . .
  );
  port (
    port_declaration;
    port_declaration;
    . . .
  );
end component;
    
```

- E.g., a decade (mod-10) counter

```

entity dec_counter is
  port (
    clk, reset: in std_logic;
    en: in std_logic;
    q: out std_logic_vector(3 downto 0);
    pulse: out std_logic
  );
end dec_counter;
    
```


```

architecture up_arch of dec_counter is
  signal r_reg: unsigned(3 downto 0);
  signal r_next: unsigned(3 downto 0);
  constant TEN: integer := 10;
begin
  -- register
  process(clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others >> '0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
  -- next-state logic
  process(en, r_reg)
  begin
    r_next <= r_reg;
    if (en='1') then
      if r_reg=(TEN-1) then
        r_next <= (others >> '0');
      else
        r_next <= r_reg + 1;
      end if;
    end if;
  end process;
  -- output logic
  q <= std_logic_vector(r_reg);
  pulse <= '1' when r_reg=(TEN-1) else
    '0';
end up_arch;
    
```

- Component declaration for dec\_counter

```

 component dec_counter
  port (
    clk, reset: in std_logic;
    en: in std_logic;
    q: out std_logic_vector(3 downto 0);
    pulse: out std_logic
  );
end component;
    
```



## Component instantiation

- Instantiate an instance of a component
- Provide a generic value
- Map formal signals to actual signals


## • Syntax

```
instance_label: component_name
  generic map(
    generic_association;
    generic_association;
    . . .
  )
  port map(
    port_association;
    port_association;
    . . .
  );
```

- Port association (named association)

```
port_name => signal_name
```

 - E.g., 2-digit decimal counter  
(00=>01=> . . . =>99 =>00 . . .)



```
library ieee;
use ieee.std_logic_1164.all;
entity hundred_counter is
  port(
    clk, reset: in std_logic;
    en: in std_logic;
    q_ten, q_one: out std_logic_vector(3 downto 0);
    p100: out std_logic
  );
end hundred_counter;
```

```
architecture vhdl_87_arch of hundred_counter is
  component dec_counter
  port(
    clk, reset: in std_logic;
    en: in std_logic;
    q: out std_logic_vector(3 downto 0);
    pulse: out std_logic
  );
  end component;
  signal p_one, p_ten: std_logic;
```

```
begin
  one_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>en,
              pulse=>p_one, q=>q_one);
  ten_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>p_one,
              pulse=>p_ten, q=>q_ten);
  p100 <= p_one and p_ten;
end vhdl_87_arch;
```

- The VHDL code is a textual description of a schematic

## • Positional association

- Appeared to be less cumbersome
- E.g., order of port declaration in entity:


```
clk, reset, en, q, pulse
```

- Alternative component instantiation

```
one_digit: dec_counter
  port map (clk, reset, en, q_one, p_one);
ten_digit: dec_counter
  port map (clk, reset, p_one, q_ten, p_ten);
```

- Trouble if the order later changes in entity declaration

 - Mapping of constant and unused port
  - E.g.,



```

one_digit: dec_counter
  port map (clk=>clk, reset=>reset, en=>'1',
           pulse=>p_one, q=>q_one);
ten_digit: dec_counter
  port map (clk=>clk, reset=>reset, en=>p_one,
           pulse=>open, q=>q_ten);

```

- Good synthesis software should
  - remove the unneeded part
  - perform optimization over the constant input

### 3. Generics

- Mechanism to pass info into an entity/component
- Declared in entity declaration and then can be used as a constant in port declaration and architecture body
- Assigned a value when the component is instantiated.
- Like a parameter, but has to be constant

- e.g., parameterized binary counter
  - Note that the generic is declared before the port and thus can be used in port declaration

```

entity para_binary_counter is
  generic (WIDTH: natural);
  port (
    clk, reset: in std_logic;
    q: out std_logic_vector(WIDTH-1 downto 0)
  );
end para_binary_counter;

```

```

architecture arch of para_binary_counter is
  signal r_reg, r_next: unsigned(WIDTH-1 downto 0);
begin
  process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
  r_next <= r_reg + 1;
  q <= std_logic_vector(r_reg);
end arch;

```

- e.g., to use the parameterized counter

```

library ieee;
use ieee.std_logic_1164.all;
entity generic_demo is
  port (
    clk, reset: in std_logic;
    q_4: out std_logic_vector(3 downto 0);
    q_12: out std_logic_vector(11 downto 0)
  );
end generic_demo;

```

```

architecture vhdl_87_arch of generic_demo is
  component para_binary_counter
    generic (WIDTH: natural);
    port (
      clk, reset: in std_logic;
      q: out std_logic_vector(WIDTH-1 downto 0)
    );
  end component;
begin
  four_bit: para_binary_counter
    generic map (WIDTH=>4)
    port map (clk=>clk, reset=>reset, q=>q_4);
  twe_bit: para_binary_counter
    generic map (WIDTH=>12)
    port map (clk=>clk, reset=>reset, q=>q_12);
end vhdl_87_arch;

```

- e.g., parameterized mod-n counter
  - Count from 0 to n-1 and wrap around
  - Note that WIDTH depends on N

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity mod_n_counter is
  generic (
    N: natural;
    WIDTH: natural
  );
  port (
    clk, reset: in std_logic;
    en: in std_logic;
    q: out std_logic_vector(WIDTH-1 downto 0);
    pulse: out std_logic
  );
end mod_n_counter;


```

```

architecture arch of mod_n_counter is
  signal r_reg: unsigned(WIDTH-1 downto 0);
  signal r_next: unsigned(WIDTH-1 downto 0);
begin
  -- register
  process(clk, reset)
  begin
    if (reset='1') then
      r_reg <= (others>>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
  -- next-state logic
  process(en, r_reg)
  begin
    r_next <= r_reg;
    if (en='1') then
      if r_reg=(N-1) then
        r_next <= (others>>'0');
      else
        r_next <= r_reg + 1;
      end if;
    end if;
  end process;
  -- output logic
  q <= std_logic_vector(r_reg);
  pulse <= '1' when r_reg=(N-1) else
    '0';
end arch;

```

 - E.g., the 2-digit decimal counter again



```

one_digit: mod_n_counter
  generic map (N=>10, WIDTH=>4)
  port map (clk=>clk, reset=>reset, en=>en,
    pulse=>p_one, q=>q_one);
ten_digit: mod_n_counter
  generic map (N=>10, WIDTH=>4)
  port map (clk=>clk, reset=>reset, en=>p_one,
    pulse=>p_ten, q=>q_ten);
p100 <= p_one and p_ten;

```



- Another useful application of generic: passing delay information

$y \leq a + b$  after  $T_{pd}$  ns;
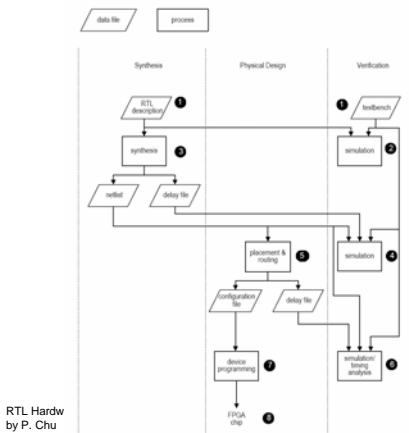 
## 4. Configuration

- Bind a component with an entity and an architecture
- Flexible and involved.
- Only simple binding of entity and architecture is needed in synthesis
  - Entity: like a socket in a printed circuit board
  - Architecture: like an IC chip with same outline
- Not supported by all synthesis software

- Application of binding:
  - E.g., adder with different speed:  
Fast but large adder or small but slow adder
  - E.g., Test bench descriptions at different stages



- Type of configuration:
  - Configuration declaration (an independent design unit)
  - Configuration specification (in architecture body)
- Default binding: (no configuration)
  - Component bound to an entity with identical name
  - Component ports bound to entity ports of same names
  - Most recently analyzed architecture body bound to the entity

- Configuration declaration
  - An independent design unit
  - Simplified syntax

```

configuration conf_name of entity_name is
  for architecture_name
    for instance_label: component_name
      use entity lib_name.bound_entity_name(bound_arch_name);
    end for;
    for instance_label: component_name
      use entity lib_name.bound_entity_name(bound_arch_name);
    end for;
  end for;
end;
  
```

- E.g., create two architecture bodies for the decade counter (one up and one down)

```

architecture down_arch of dec_counter is
  -- next-state logic
  process(en,r_reg)
  begin
    r_next <= r_reg;
    if (en='1') then
      if r_reg=0 then
        r_next <= to_unsigned(TEN-1,4);
      else
        r_next <= r_reg - 1;
      end if;
    end if;
  end process;
  -- output logic
  q <= std_logic_vector(r_reg);
  pulse <= '1' when r_reg=0 else
           '0';
  
```

```

library ieee;
use ieee.std_logic_1164.all;
entity hundred_counter is
  port(
    clk, reset: in std_logic;
    en: in std_logic;
    q_ten, q_one: out std_logic_vector(3 downto 0);
    p100: out std_logic
  );
end hundred_counter;
begin
  one_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>en,
              pulse=>p_one, q=>q_one);
  ten_digit: dec_counter
    port map (clk=>clk, reset=>reset, en=>p_one,
              pulse=>p_ten, q=>q_ten);
  p100 <= p_one and p_ten;
end vhdl_87_arch;

```

RTL Hardware Design  
by P. Chu

Chapter 13

37

```

configuration count_down_config of hundred_counter is
  for vhdl_87_arch
    for one_digit: dec_counter
      use entity work.dec_counter(down_arch);
    end for;
    for ten_digit: dec_counter
      use entity work.dec_counter(down_arch);
    end for;
  end for;
end;

```

RTL Hardware Design  
by P. Chu

Chapter 13

38

- Configuration specification
  - Included in the declaration section of architecture body

- Syntax:

```

for instance_label: component_name
  use entity lib_name.bound_entity_name(bound_arch_name);
for instance_label: component_name
  use entity lib_name.bound_entity_name(bound_arch_name);

```

RTL Hardware Design  
by P. Chu

Chapter 13

39

- E.g.,

```

architecture vhdl_87_config_arch of hundred_counter is
  component dec_counter
    port(
      clk, reset: in std_logic;
      en: in std_logic;
      q: out std_logic_vector(3 downto 0);
      pulse: out std_logic
    );
  end component;
  for one_digit: dec_counter
    use entity work.dec_counter(down_arch);
  for ten_digit: dec_counter
    use entity work.dec_counter(down_arch);
  signal p_one, p_ten: std_logic;
begin

```

RTL Hardware Design  
by P. Chu

Chapter 13

40

- Component instantiation and configuration in VHDL 93

- Remove component and configuration declaration
- Usually satisfactory for RT-level synthesis
- Syntax:

```

instance_label:
  entity lib_name.bound_entity_name(bound_arch_name)
  generic map (. . .)
  port map (. . .);

```

RTL Hardware Design  
by P. Chu

Chapter 13

41

- E.g.,

```

architecture vhdl_93_arch of hundred_counter is
  signal p_one, p_ten: std_logic;
begin
  one_digit: entity work.dec_counter(up_arch)
    port map (clk=>clk, reset=>reset, en=>en,
              pulse=>p_one, q=>q_one);
  ten_digit: entity work.dec_counter(up_arch)
    port map (clk=>clk, reset=>reset, en=>p_one,
              pulse=>p_ten, q=>q_ten);
  p100 <= p_one and p_ten;
end vhdl_93_arch;

```

RTL Hardware Design  
by P. Chu

Chapter 13

42

## 5. Other constructs for developing large system

- Library
- Subprogram
- Package

## Library

- A virtual repository to stored analyzed design units
- Physical location determined by software
- Design units can be organized and stored in different libraries

- Default library: work
  - E.g.,

```
one_digit: entity work.dec_counter(up_arch)
```

- Non-default library has to be declared:
  - syntax:

```
library lib_name, lib_name, ... , lib_name;
```

- E.g., library ieee;

- E.g.,

```
library c_lib; -- make c_lib visible
configuration clib_config of hundred_counter is
  for vhdl_87_arch
    for one_digit: dec_counter
      use entity c_lib.dec_counter(down_arch); -- c_lib
    end for;
    for ten_digit: dec_counter
      use entity c_lib.dec_counter(down_arch); -- c_lib
    end for;
  end for;
end;
```

## Subprogram

- Include function and procedure
- Made of sequential statement
- Is not a design unit; must be declared
- Aimed for software hierarchy not hardware hierarchy
- We only use function
  - Shorthand for complex expression
  - “House-keeping tasks; e.g., type conversion

- Syntax of function

```
function func_name(parameter_list) return data_type is
  declarations;
begin
  sequential statement;
  sequential statement;
  . . .
  return (expression);
end;
```



- E.g.,

```
architecture arch of . . .
  -- declaration
  function maj(a, b, c: std_logic) return std_logic is
    variable result: std_logic;
  begin
    result := (a and b) or (a and c) or (b and c);
    return result;
  end maj;
  signal i1, i2, i3, i4, x, y: std_logic;
begin
  . . .
  x <= maj(i1, i2, i3) or i4;
  y <= i1 when maj(i2, i3, i4)='1' else
  . . .
```

- E.g.,

```
function to_boolean(a: std_logic) return boolean is
  variable result: boolean;
begin
  if a='1' then
    result := true;
  else
    result := false;
  end if;
  return result;
end to_boolean;
```

- E.g.,  $\lceil \log_2 n \rceil$

```
function log2c(n: integer) return integer is
  variable m, p: integer;
begin
  m := 0;
  p := 1;
  while p < n loop
    m := m + 1;
    p := p * 2;
  end loop;
  return m;
end log2c;
```

## Package

- Organize and store declaration information, such as data types, functions etc.
- Divided into
  - Package declaration
  - Package body (implementation of subprograms)
- Both are design units

- Syntax

```
package package_name is
  declaration item;
  declaration item;
  . . .
end package_name;
```

```
package body package_name is
  subprogram;
  subprogram;
  . . .
end package_name;
```

- E.g.,

```
-- package declaration
library ieee;
use ieee.std_logic_1164.all;
package util_pkg is
  type std_logic_2d is
    array(integer range <>, integer range <>) of std_logic;
  function log2c (n: integer) return integer;
end util_pkg ;
```

```

--package body
package body util_pkg is
  function log2c(n: integer) return integer is
    variable m, p: integer;
  begin
    m := 0;
    p := 1;
    while p < n loop
      m := m + 1;
      p := p * 2;
    end loop;
    return m;
  end log2c;
end util_pkg;

```

- Improved mod-n counter

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use work.util_pkg.all;
entity better_mod_n_counter is
  generic(N: natural);
  port(
    clk, reset: in std_logic;
    en: in std_logic;
    q: out std_logic_vector(log2c(N)-1 downto 0);
    pulse: out std_logic
  );
end better_mod_n_counter;

architecture arch of better_mod_n_counter is
  constant WIDTH: natural := log2c(N);
  signal r_reg: unsigned(WIDTH-1 downto 0);
  signal r_next: unsigned(WIDTH-1 downto 0);
begin

```

## 6. Partition

- Physical partition:
  - Division of the physical implementation
  - Each subsystem is synthesized independently
  - Partition too small: loose optimization opportunity
  - Partition too large: require too much resource
    - e.g.,  $O(n^3)$  algorithm 1000 gates for 1 sec;
    - 35 hours ( $50^3$  sec) for one 50,000 gate circuit
    - 21 min ( $10 \cdot 5^3$  sec) for 10 5,000 gate circuit
  - 5000 to 50,000 gates for today's synthesizer

- Logical partition:
  - Help development and verification process for human designers
  - Logical partitions can be merged later in synthesis
- Some circuit should be isolated as independent modules
  - Device-dependent circuit: e.g., memory modules
  - “Non-Boolean” circuit: tri-state buffer, delay-sensitive circuit, clock distribution network, synchronization circuit.